

**CONTINUOUS INTERNAL EVALUATION - 2**

Dept: EC	Sem / Div: I/ABC	Sub: Basic Electrical Engineering	S Code:21ELE13
Date:17/02/22	Time: 3:00-4:30	Max Marks: 40	Elective: N

Note: Answer any 2 full questions, choosing one full question from each part.

QN	Questions	Marks	RBT	CO's
<b>PART A</b>				
1 a	Two circuits A and B are connected in parallel across 200V, 50Hz supply. Circuit A consist of $10\Omega$ resistance and $0.12H$ inductance in series while circuit B consist of $20\Omega$ resistance in series with $40\mu F$ capacitance. Calculate i) Current in circuit and B ii) Total current iii) Total power	8	L3	CO1
b	Show that two wattmeters are sufficient to measure three phase power for 3 phase balanced circuit.	6	L2	CO1
c	In three phase star connection find the relation between line and phase values of current and voltage. Also derive the equation for three phase power.	6	L3	CO1
<b>OR</b>				
2 a	A balanced three phase star connected load draws power from 440V supply. The two wattmeter connected indicated $W1=750W$ and $W2=1.5KW$ . Calculate power, power factor and current in the circuit. If the $W1$ wattmeter is reserved, what would be the phase angle between voltage and current.	8	L3	CO1
b	A balanced delta connected load of $8+j6$ per phase is connected to a 3 phase 230V, 50Hz voltage supply, find i) phase current ii) line current iii) power factor	6	L3	CO1

	iv) power v) reactive power vi) volt ampere			
	c What is advantage of high voltage transmission.	6	L2	CO3
<b>PART B</b>				
3	a Three coil each having resistance of $10\Omega$ and inductance of $0.02H$ are connected in star across $440V, 50Hz$ 3phase supply. Calculate the line current and total power consumed.	6	L3	CO1
	b Define earthing. Why is earthing required? Explain pipe earthing with diagram	8	L2	CO4
	c Mention the relative advantage and disadvantage of overhead lines and underground cables for distribution of electrical energy.	6	L2	CO3
<b>OR</b>				
4	a Write the difference between Fuse and MCB.	5	L2	CO4
	b Calculate the electricity bill amount for a month of 31 days, if the following devices are used as specified. (A) 3 bulbs of $40W$ for 6 hours (B) 4 tube lights of $50W$ for 8 hours (C) A T.V. of $120W$ for 6 hours Given the rate of electricity is Rs. 2.50 per unit	5	L3	CO4
	c A voltage $V=100 \sin 314t$ is applied to a circuit consisting of a $25\Omega$ resistor and an $80\mu F$ capacitor in series. Determine i) peak value of current ii) Power factor iii) Total power consumed by the circuit. iv) find the components of the power triangle.	10	L3	CO1

*Somya Anil*  
Prepared by: *Mrs Somya*

*S. hat*  
HOD